



### **Features**

- 400 watts peak pulse power (t p = 8/20µs)
- Protects two -7V to 12V lines
- Low capacitance
- Low clamping voltage
- Solid -state silicon avalanche technology
- IEC 61000-4-2 Level 4 (±8kV contact ±15kV air)


## **Applications**

- Protection of RS -485 transceivers with extended common -mode range
- Security systems
- Automatic Teller Machines
- HFC systems
- Net works





Marking: 7AM SOT-23

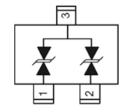

**Schematic Diagram** 

Absolute Maximum Ratings ( Ta=25℃ unless otherwise noted )				
Parameter	Symbol	Value	Units	
Peak Pulse Power	P <sub>PP</sub> <sup>(1)</sup>	400	W	
Peak Pulse Current	I <sub>PP</sub> (1)	12	А	
Lead Solder Temperature – Maximum (10 Second Duration)	TL	260		
Junction Temperature	T <sub>J</sub>	-55 to 125	$^{\circ}$	
Storage Temperature	T <sub>STG</sub>	-55 to 150		

Note: 1 Non-repetitive current pulse 8/20 µs exponential decay waveform according to IEC61000-4-5.

		Test Condition	less otherwise specified ) Pins 1 to 3 and 2 to 3		Pins 3 to 1 and 3 to		Unit		
Parameter	Symbol		(12V TVS)		2(7V TVS)				
			Min	Тур.	Max	Min	Тур.	Max	
Reverse standoff voltage	V <sub>RWM</sub>	Pin 3 to 1 or Pin 2 to 1			12			7	V
Breakdown voltage	V <sub>BR</sub>	Iτ=1mA	13.3			7.5			V
Reverse leakage current	I <sub>R</sub>	VR= VRWM			1			1	μΑ
Clamping voltage Vc	$I_{PP}=5A$ , $t_p=8/20\mu s$			20			10	V	
	VC	I <sub>PP</sub> =12Α, t <sub>p</sub> = 8/20μs			26				V
Junction	Сл	V <sub>R</sub> =0V,f=1MHz			75			75	~ F
capacitance		V <sub>R</sub> =0V,f=1MHz		45			45		pF



### **Ratings and Characteristics Curves**

(TA = 25°C unless otherwise noted)

Figure 1 Non-Repetitive Peak Pulse Power vs. Pulse Time

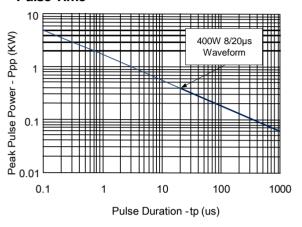


Figure 2 Power Derating curve

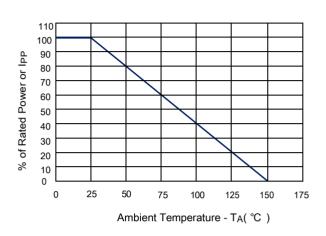


Figure 3 Pulse Waveform

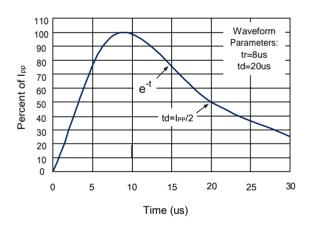


Figure 4 Clamping Voltage vs. Peak Pulse Current


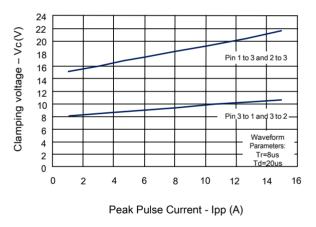


Figure 5 Capacitance vs. Reverse Voltage

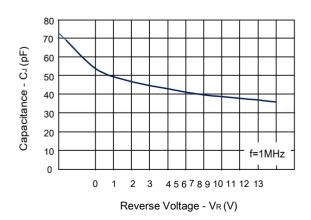




## **Application Information**


#### **Device Connection for Protection of Two RS-485 Data Lines**

EIA RS-485 specifies a  $\pm 7V$  ground difference between devices on the bus. This permits the bus voltage to range from +12V (5V + 7V) to -7V (0 - 7V).

#### **RS-485 Common Mode Voltages**

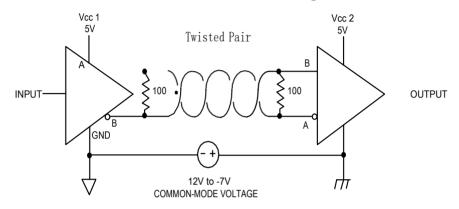


#### **RS-485 Protection Circuit**

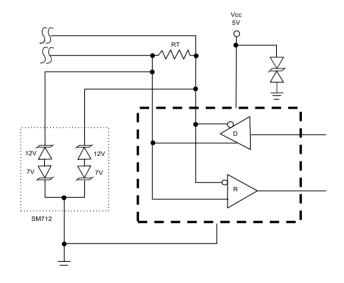





# Package Outline Dimensions

in inches (millimeters)

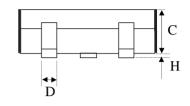

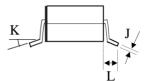

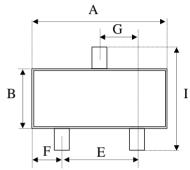

Dim	millmeters		
Dilli	min	max	
Α	2.80	3.00	
В	1.20	1.40	
С	0.89	1.11	
D	0.30	0.50	
Е	1.78	2.04	
F	0.45	0.60	
G	0.89	1.02	
Н	0.013	0.100	
I	2.25	2.55	
J	0.085	0.177	
K	0° 10°		
L	0.45 0.60		

# **Revision History**

Document Version	Date of release	Discroption of changes
Rev.A	2014.03.25	First issue



#### **Disclaimers**

These materials are intended as a reference to assist our customers in the selection of the Suzhou Good-Ark product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Suzhou Good-Ark Electronics Co., Ltd.or a third party.

Suzhou Good-Ark Electronics Co., Ltd. assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.

All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Suzhou Good-Ark Electronics Co., Ltd. without notice due to product improvements or other reasons. It is therefore recommended that customers contact Suzhou Good-Ark Electronics Co., Ltd. or an authorized Suzhou Good-Ark Electronics Co., Ltd. for the latest product information before purchasing a product listed herein. The information described here may contain technical inaccuracies or typographical errors. Suzhou Good-Ark Electronics Co., Ltd. assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors. Please also pay attention to information published by Suzhou Good-Ark Electronics Co., Ltd. by various means, including our website home page. (http://www.goodark.com)

When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, Please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Suzhou Good-Ark Electronics Co., Ltd. assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.

The prior written approval of Suzhou Good-Ark Electronics Co., Ltd. is necessary to reprint or reproduce in whole or in part these materials.

Please contact Suzhou Good-Ark Electronics Co., Ltd. or an authorized distributor for further details on these materials or the products contained herein.